

Gate Level Modeling Part-II

Feb-9-2014

Always hit the target
with SmartDV Verification Services



- Verilog
- Tutorial
- Examples
- Questions
- Tools
- Books
- Links
- FAQ


- Sponsor
- Home
- Disclaimer
- FAQ



● Designing Using Primitives

Designing using primitives is used only in library development, where the ASIC vendor provides the ASIC library Verilog description, using Verilog primitives and user defined primitives (UDP).

❖ AND Gate from NAND Gate

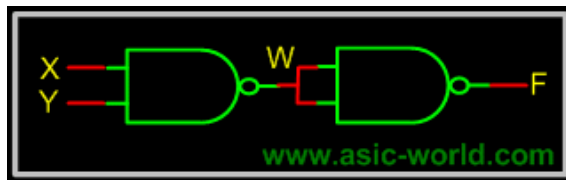

✦ Code

```

1 // Structural model of AND gate from two NANDS
2 module and_from_nand();
3
4 reg X, Y;
5 wire F, W;
6 // Two instantiations of the module NAND
7 nand U1(W,X, Y);
8 nand U2(F, W, W);
9
10 // Testbench Code
11 initial begin
12     $monitor ("X = %b Y = %b F = %b", X, Y, F);
13     X = 0;
14     Y = 0;
15     #1 X = 1;
16     #1 Y = 1;
17     #1 X = 0;
18     #1 $finish;
19 end
20
21 endmodule

```


You could download file and_from_nand.v [here](#)

```

X = 0 Y = 0 F = 0
X = 1 Y = 0 F = 0
X = 1 Y = 1 F = 1
X = 0 Y = 1 F = 0

```

❖ D-Flip flop from NAND Gate

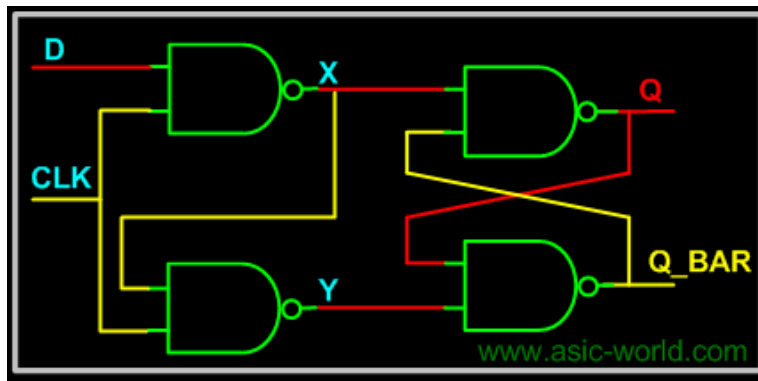

✦ Verilog Code

```

1 module dff_from_nand();
2 wire Q,Q_BAR;
3 reg D,CLK;
4
5 nand U1 (X,D,CLK) ;
6 nand U2 (Y,X,CLK) ;
7 nand U3 (Q,Q_BAR,X);
8 nand U4 (Q_BAR,Q,Y);
9
10 // Testbench of above code
11 initial begin
12     $monitor("CLK = %b D = %b Q = %b Q_BAR = %b",CLK, D, Q, Q_BAR);
13     CLK = 0;
14     D = 0;
15     #3 D = 1;
16     #3 D = 0;
17     #3 $finish;
18 end
19
20 always #2 CLK = ~CLK;
21
22 endmodule

```


You could download file dff_from_nand.v [here](#)

```

CLK = 0 D = 0 Q = x Q_BAR = x
CLK = 1 D = 0 Q = 0 Q_BAR = 1
CLK = 1 D = 1 Q = 1 Q_BAR = 0
CLK = 0 D = 1 Q = 1 Q_BAR = 0
CLK = 1 D = 0 Q = 0 Q_BAR = 1
CLK = 0 D = 0 Q = 0 Q_BAR = 1

```

✦ Multiplexer from primitives

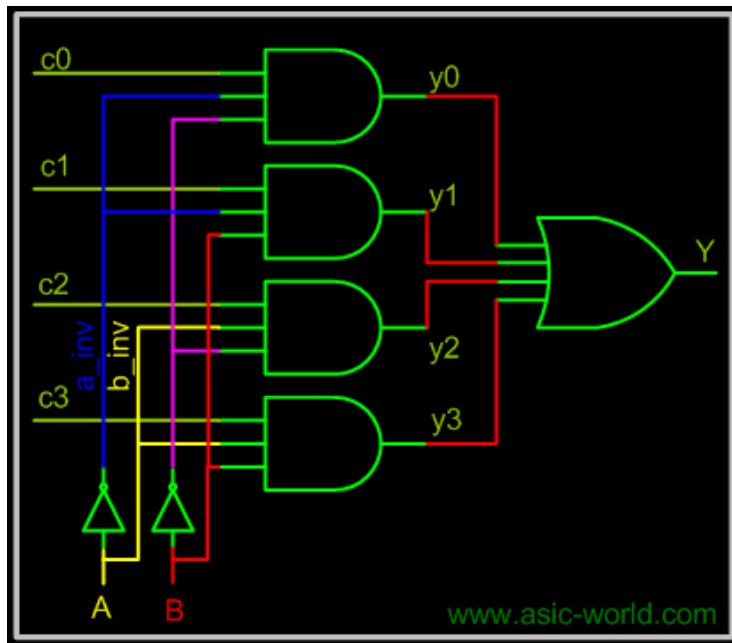

◆ Verilog Code

```

1 module mux_from_gates ();
2 reg c0,c1,c2,c3,A,B;
3 wire Y;
4 //Invert the sel signals
5 not (a_inv, A);
6 not (b_inv, B);
7 // 3-input AND gate
8 and (y0,c0,a_inv,b_inv);
9 and (y1,c1,a_inv,B);
10 and (y2,c2,A,b_inv);
11 and (y3,c3,A,B);
12 // 4-input OR gate
13 or (Y, y0,y1,y2,y3);
14
15 // Testbench Code goes here
16 initial begin
17     $monitor (
18         "c0 = %b c1 = %b c2 = %b c3 = %b A = %b B = %b Y = %b",
19         c0, c1, c2, c3, A, B, Y);
20     c0 = 0;
21     c1 = 0;
22     c2 = 0;
23     c3 = 0;
24     A = 0;
25     B = 0;
26     #1 A = 1;
27     #2 B = 1;
28     #4 A = 0;
29     #8 $finish;
30 end
31
32 always #1 c0 = ~c0;
33 always #2 c1 = ~c1;
34 always #3 c2 = ~c2;
35 always #4 c3 = ~c3;
36
37 endmodule

```

You could download file mux_from_gates.v [here](#)

```
c0 = 0 c1 = 0 c2 = 0 c3 = 0 A = 0 B = 0 Y = 0
c0 = 1 c1 = 0 c2 = 0 c3 = 0 A = 1 B = 0 Y = 0
c0 = 0 c1 = 1 c2 = 0 c3 = 0 A = 1 B = 0 Y = 0
c0 = 1 c1 = 1 c2 = 1 c3 = 0 A = 1 B = 1 Y = 0
c0 = 0 c1 = 0 c2 = 1 c3 = 1 A = 1 B = 1 Y = 1
c0 = 1 c1 = 0 c2 = 1 c3 = 1 A = 1 B = 1 Y = 1
c0 = 0 c1 = 1 c2 = 0 c3 = 1 A = 1 B = 1 Y = 1
c0 = 1 c1 = 1 c2 = 0 c3 = 1 A = 0 B = 1 Y = 1
c0 = 0 c1 = 0 c2 = 0 c3 = 0 A = 0 B = 1 Y = 0
c0 = 1 c1 = 0 c2 = 1 c3 = 0 A = 0 B = 1 Y = 0
c0 = 0 c1 = 1 c2 = 1 c3 = 0 A = 0 B = 1 Y = 1
c0 = 1 c1 = 1 c2 = 1 c3 = 0 A = 0 B = 1 Y = 1
c0 = 0 c1 = 0 c2 = 0 c3 = 1 A = 0 B = 1 Y = 0
c0 = 1 c1 = 0 c2 = 0 c3 = 1 A = 0 B = 1 Y = 0
c0 = 0 c1 = 1 c2 = 0 c3 = 1 A = 0 B = 1 Y = 1
```



Copyright © 1998-2014

Deepak Kumar Tala - All rights reserved

Do you have any Comment? mail me at: deepak@asic-world.com